
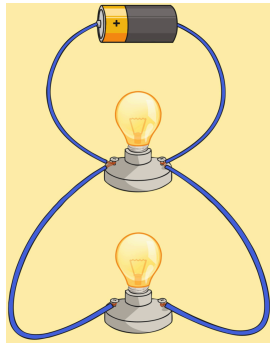


# Battery Operated Lights


Parallel

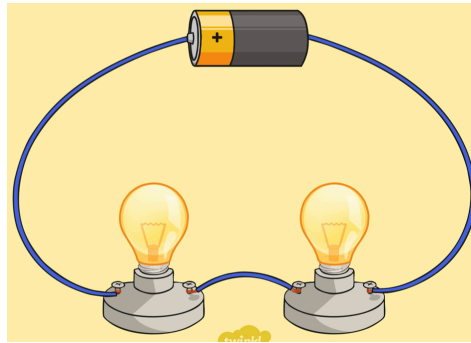


Series circuit



Circuit

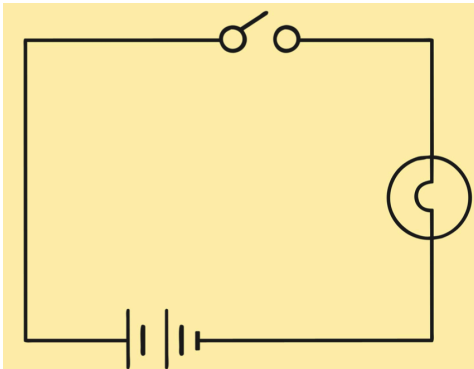

Electrical system

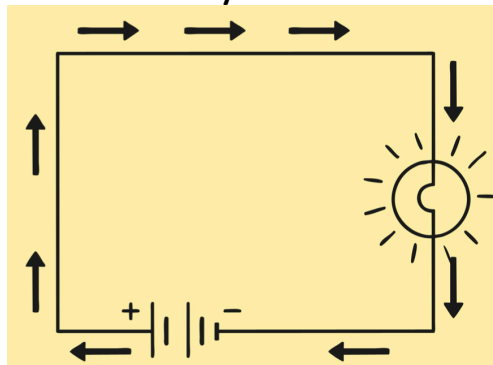


Evaluate


Does my lamp...

- Appeal to children
- Look colourful
- Give a bright light
- Have an easy to use switch

Insulator

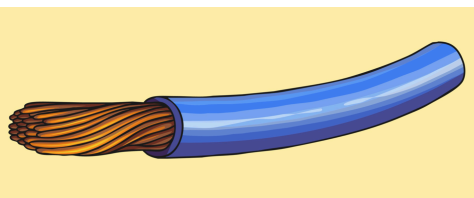


Conductor

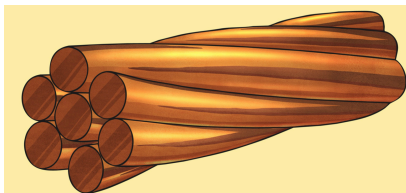

Component

Bulb		
Motor		
Battery		
Switch		
Buzzer		


Symbol

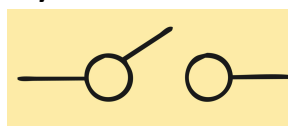

Functional



Mains

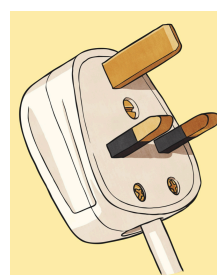

Battery

